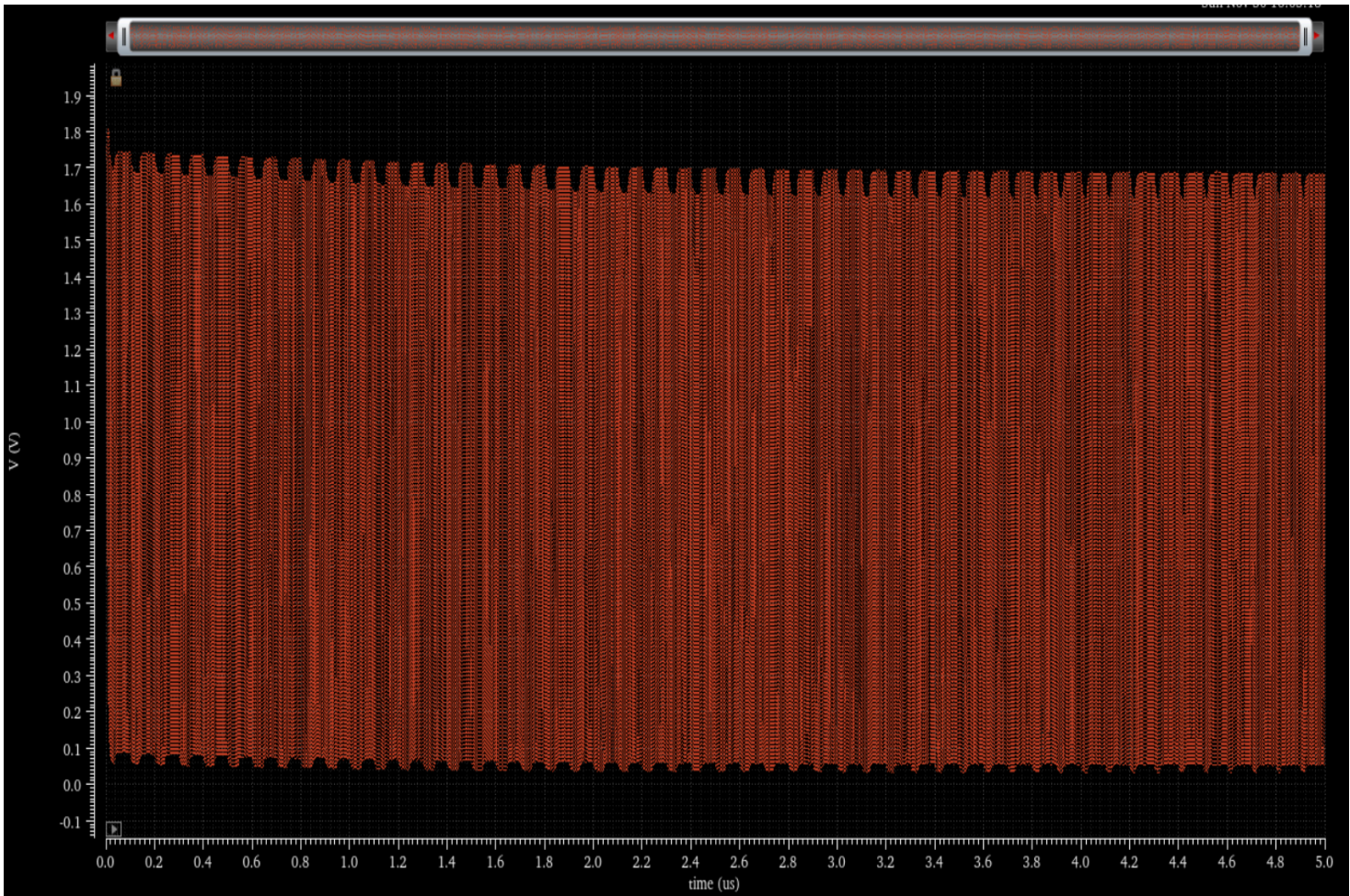


PLL SIMULATION RESULTS :(5 micro seconds)


OUTPUT AT VCO :



FREQUENCY OUTPUT OF VCO :

Outputs				
	Name/Signal/Expr	Value	Plot	Save
1	frequency(v("/net8" ?result "tran"))	1.20418G	☒	☐
2	net8		☒	☐
3	net7		☒	☐

V CONTROL PLOT FOR 5 micro seconds :

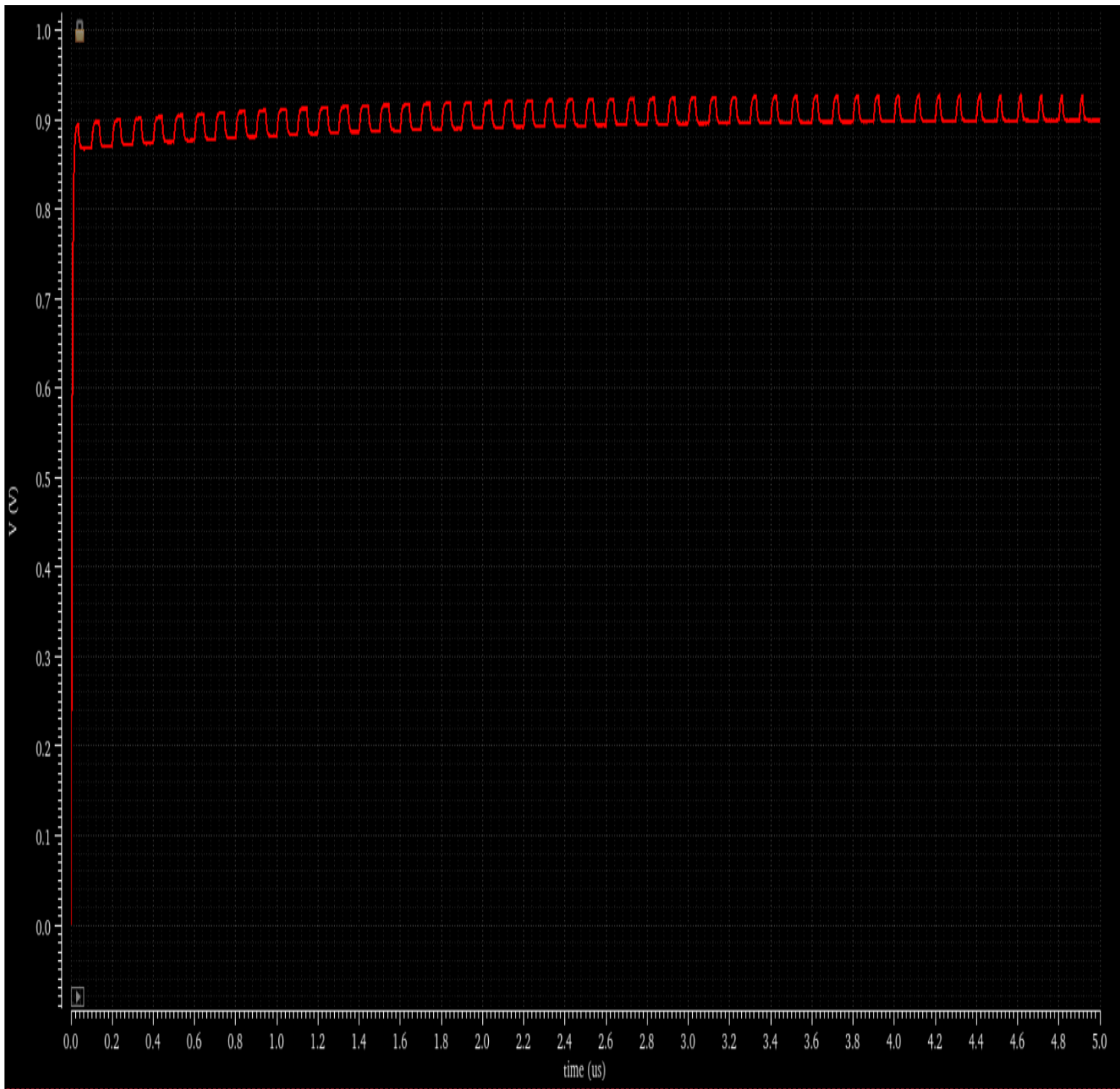

Plots for UP(Orange), Down(Green) and Divider output(Purple) signals :

